

ECEN 704 VLSI Circuit Design Project

Name: Yu-Hao Chen, UIN:435009528

1. Introduction

Design a Fully Differential Folded Cascode Amplifier (FDCA) with common mode feedback (CMFB) and a wide-swing current mirror bias circuit, adhering to the following design specifications.

DESIGN SPECIFICATIONS

| Tech | IBM180nmCMOS | | |
|---------|-----------------------------------|-------------------------------|-------|
| | Specification | Value | loop |
| VDD | Supply voltage | 1.8v | |
| VCM | Common-modelevel | 0.9v | |
| Power | Power dissipation | $\leq 3\text{mW}$ | Open |
| Gain | DCgain | $\geq 60\text{dB}$ | Open |
| GBW | Gain Band Width | $\geq 120\text{MHz}$ | Open |
| SR | Slew rate | $\geq 75\text{V}/\mu\text{s}$ | Open |
| Noise | Input-referred noise (1Hz-100MHz) | $\leq 50\mu\text{Vrms}$ | Open |
| PM | Differential phase margin | $\geq 60^\circ$ | Close |
| CMFB PM | CMFB phase margin | $\geq 60^\circ$ | Close |
| IM3 | IM3(1Vpp@1MHz) | $\leq -60\text{dB}$ | Close |
| Area | Chip area (including pads) | 1mm \times 1mm | |

2. Design Procedure

2-1 Circuit Topology

A fully differential folded cascode amplifier offers better phase margin and output swing, while a Miller OPA is preferable if need a very high gain. Also, fully differential folded cascode amplifier can omit extra capacitors and also reduces design area.

2-2 Design Calculations

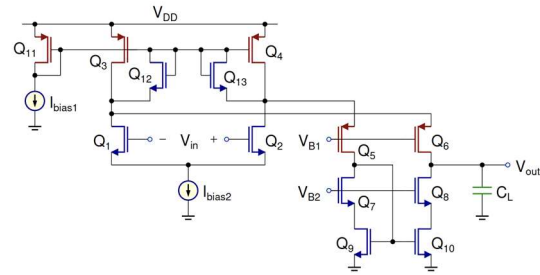


Figure 1

- To achieve the Power dissipation $\leq 3\text{mW}$ we can know that $1.8\text{v} \cdot I \leq 3\text{mW}$, $I_{\text{all}} \leq 1.66\text{mA}$
- For the SR we can first decide the current over the Q4 and Q5, $I/CL (2.5\text{p}) \geq 75\text{V}/\mu\text{s}$, $I \geq 187.5\text{mA}$. Choosing $250\mu\text{A}$ for Q4, $150\mu\text{A}$ for Q2, $100\mu\text{A}$ for Q5 Q7 Q9, $300\mu\text{A}$ for Ibais2
- Next, we can determine the W/L of the transistors by using the gm/I_d method, transconductance efficiency, provides a measure of how efficiently a transistor converts a given current (I_d) into transconductance (gm). (reference 1)

 


Figure (2-1) NMOS Id/W | gm/id

 


Figure (2-2) PMOS Id/W | gm/id

- To achieve the DC gain we choose $L=500\text{nm}$ to lower λ , higher r_{ds} .
- We require a higher transconductance (gm) for the first amplifier, Q2 NMOS, for

reduced noise and a gain-bandwidth product (GBW) of at least 120 MHz, which is defined by the condition $gm/2\pi CL \geq 120$ MHz and $gm \geq 1.884$ m. This implies that gm/Id (150 μ A) must be at least 13. For our design, we select $gm = 2.7$ m under a bias current of $I = 150$ μ A, resulting in an x-axis gm/Id of 18, a y-axis Id/W of 1.4, and a width (W) of 80.

For the other transistors, after determining the current for each transistor, we selected an NMOS with a gm/Id ratio of 8 and a PMOS with a gm/Id ratio of 4 to achieve lower power consumption.

3. SCHEMATICS AND SIMULATION RESULTS

3-1 Design Schematics and Descriptions

The complete schematic consists of three components: the bias circuit, the fully differential pair, and the common mode feedback. (Figure 3)

 


Fig 3. Full schematic

Using a PMOS wide-swing cascode current mirror in series with an NMOS wide-swing cascode current mirror, along with several dummy transistors for the bias circuit (see Figure 3-1).

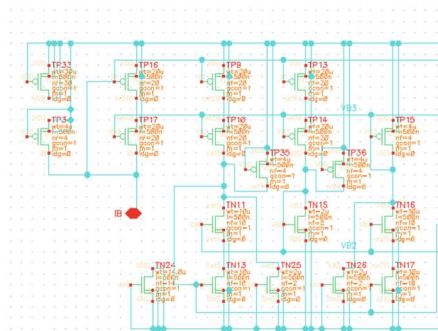


Figure 3-1

The Fully Differential Folded Cascode Amplifier (FDCA), as shown in Figure 3-2, is biased using the bias circuit.

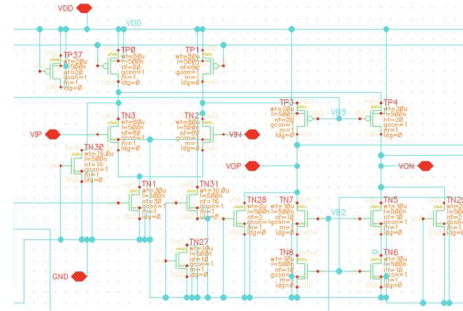


Figure 3-2

For the CMFB, decide 50uA on each side for the lower power dissipation. (Figure 3-3)

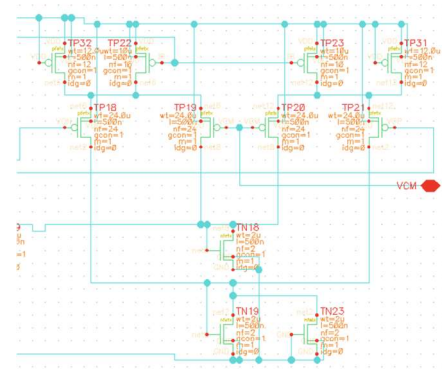


Figure 3-3

3-2 Simulation Results

Using ideal balun and some Vdc, Vsin to create open and close loop testbench

 


Figure 4 testbench

Checking dc voltage = 0.9V is in the common-mode range (0.792~1.8) that keep all transistors in active


 


Figure 5 Common-mode range

The Power dissipation is **1.8035mW**

 

DC gain (**59.3208dB**) & GBW (**128.893MHz**)
on the 0dB point (figure 5-2)

 


Figure 5-2 DC gain & GBW

Input-referred noise (1Hz-100MHz) = **52.7258u**
(Figure 5-3)

 


Figure 5-3 Input-referred noise

Slew rate = **82.89 V/μs** (figure 5-4)

 


Figure 5-4 SR

Phase margin = 180 ° - the 0dB point PM (85.91 °) = **94.09 °** (Figure 5-5)

 


Figure 5-5 PM

Phase margin for the CMFB = 180 ° - the 0dB
point PM (72.23 °) = **107.77 °** (Figure 5-6)

 


Figure 5-6 CMFB PM

0.9M(-44dB)-1M(-12dB) = **-32dB** (figure 5-7)


 


Figure 5-7 IM3


4. CHIP LAYOUT

4-1 Layout Blocks

 


4-2 Complete Chip


Chip area: **0.45u*0.38u**

 

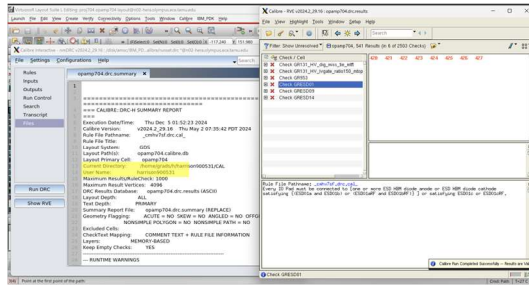4-3 DRC (with some antenna and ESD errors)




4-4 LVS

 


 5. Post layout simulation


Post layout DC gain **(59.19dB)** & GBW **(121.108MHz)**




Post layout noise = **51.8u**

 


Power post layout = **1.8mW**

 


SR post layout = **79.7V/μs**

 


PM post layout= 180-84.6= **95.4**

 

 Comparing CMFB phase margin by ringing in the step response which related to the phase margin.



IM3 (-45) -(-12) = **-33dB**

 

6. Conclusion

| | specifications | Post layout |
|---------|----------------|-------------|
| DC gain | ≥60dB | 59.19dB |
| GBW | ≥120MHz | 121.108MHz |
| Noise | ≤ 50μVrms | 51.8u |
| Power | ≤3mW | 1.8mW |
| SR | ≥75V/μs | 79.7 V/μs |
| PM | ≥60° | 95.4 |
| IM3 | ≤-60dB | -33dB |

The advantage of FDFC lies in its stability; however, having a large proportional gain (PM) can result in a slow system response, which may pose issues in certain situations.

7. Reference

[1] N. Bako1, Ž. Butkovi 2 and A. Bari 2 1Systemcom Ltd., Zagreb, Croatia- Design of Fully Differential Folded Cascode Operational Amplifier by the gm/ID Methodology
<https://www.edaboard.com/attachments/05533393-pdf.50616/>