

# 24 Fall ECEN 704: VLSI Circuit Design

## Design Pre-lab Report

### Lab8: Operational Transconductance Amplifiers

Name: Yu-Hao Chen

UIN:435009528

Section:601

Professor: Aydin Karsilayan

TA: Troy Buhr

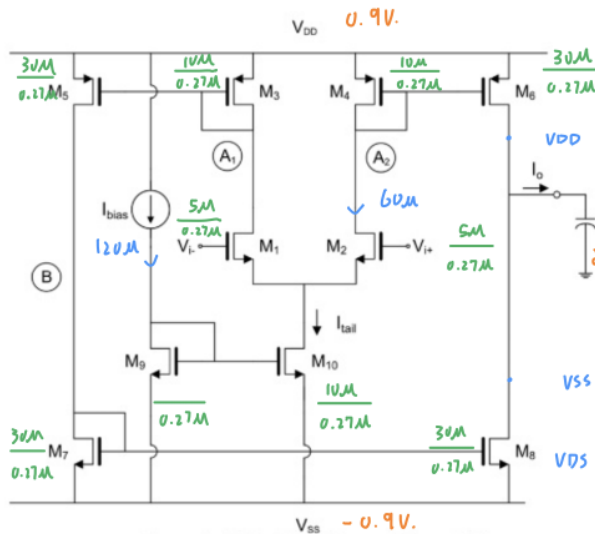


Figure 8-4: The Three Current-Mirror OTA

$G_m$	$> 500 \mu A/V$
Slew Rate	$> 10 V/\mu s$
Peak-to-Peak Output Swing	$> 1 V$
Load Capacitance	$20 pF$
Power	$< 1 mW$ (not including bias current source)
Power Supply	$V_{DD} = -V_{SS} = 0.9 V$

$$V_{SD} \geq \sqrt{\frac{N \cdot 2 I_D}{K_P \left(\frac{W}{L}\right)_6}} = 0.2$$

$$V_{DD} - 0.2 = 0.7V.$$

$$\text{Swing} = 0.7 \sim -0.7 V.$$

$$V_{SS} + 0.2 = -0.7$$

$$V_{DS} \geq \sqrt{\frac{N \cdot 2 I_D}{K_P \left(\frac{W}{L}\right)_8}} = 0.7$$

$$N = \frac{\frac{W}{L}_6}{\frac{W}{L}_4} = 3$$

$$G_m = N g_{m2} = N \left( \sqrt{2 I_D \mu_{n\text{cv}} \chi \frac{W}{L}_2} \right) > 500 \mu A/V$$

$$= 3 \times 648.91 \mu = 1.946 m$$

$$SR = N \frac{I_{tail}}{C_L} = 3 \times \frac{120}{20 p} = 18 V/\mu s$$

$$\text{Power} = 1.8 (N+1) I_{tail} < 1 mW.$$

$$1.8 \times 4 \times 120 = 0.864 mW.$$