

24 Fall ECEN 704: VLSI Circuit Design

Design Pre-lab Report

Lab7: Frequency Response of Inverting Amplifiers

Name: Yu-Hao Chen

UIN:435009528

Section:601



Professor: Aydin Karsilayan

TA: Troy Buhr

1.

	gain (M)	R _{in}	R _{out}	linearity
current mirror load	$-g_{m1} \times (r_{ds1} \parallel r_{ds2})$ medium	∞ same	$r_{ds1} \parallel r_{ds2}$ good	middle
digital cmos	$-(g_{m1} + g_{m2}) \times (r_{ds1} \parallel r_{ds2})$ good	∞ "	$r_{ds1} \parallel r_{ds2}$ good	worse
self-bias pmos	$-g_{m1} \times (\frac{1}{g_{m2}} \parallel r_{ds1})$ worse	∞ "	$r_{ds1} \parallel \frac{1}{g_{m2}}$ worse	good
self-bias cmos	$-g_{m1} \times (\frac{1}{g_{m2}} \parallel \frac{1}{g_{m2}})$ worse	∞ "	$r_{ds1} \parallel \frac{1}{g_{m2}}$ worse	middle

2.

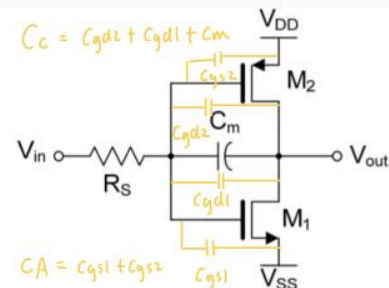
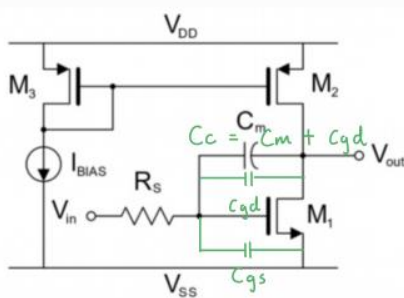


$$H(s) = \frac{V_o}{V_i} = \frac{CA + (1-M)C_c}{R_{in}} \times M \times R_{out}$$

$$R_{out} = R_B \parallel (C_B + \frac{1}{1-M} C_c)$$

$$R_{in} = R_A + (CA + (1-M) C_c)$$

	R _A	C _A	C _c	R _B	C _B
current mirror load	R _s	C _{gs1}	C _{gd1} + C _m	r _{o1} r _{o2}	C _{bd1} + C _{bd2}
digital cmos	R _s	C _{gs1} + C _{gs2}	C _{gd1} + C _{gd2} + C _m	r _{o1} r _{o2}	C _{bd1} + C _{bd2}
self-bias pmos	R _s	C _{gs1}	C _{gd1} + C _m	r _{o1} $\frac{1}{g_{m2}}$	C _{bd1} + C _{bd2} + C _{gs2}
self-bias cmos	R _s	C _{gs1}	C _{gd1} + C _m	r _{o1} $\frac{1}{g_{m2}}$	C _{bd1} + C _{bd2} + C _{gs2}

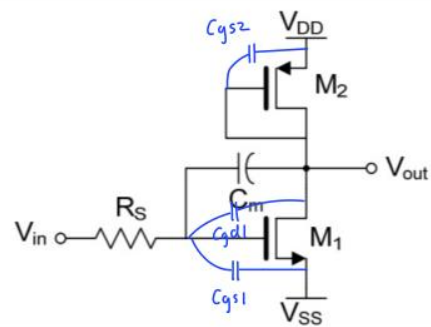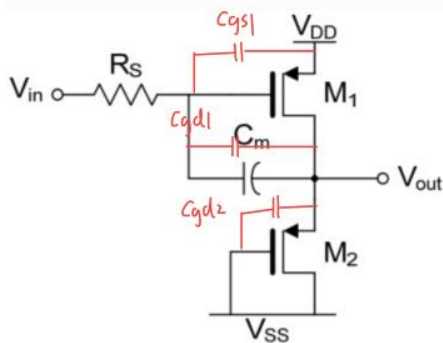

3.


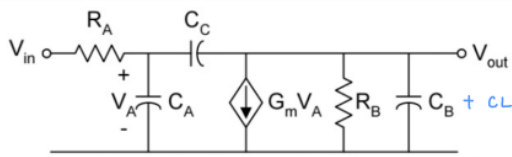


Figure 7-2: Generic Inverting Amplifier Small-Signal Model

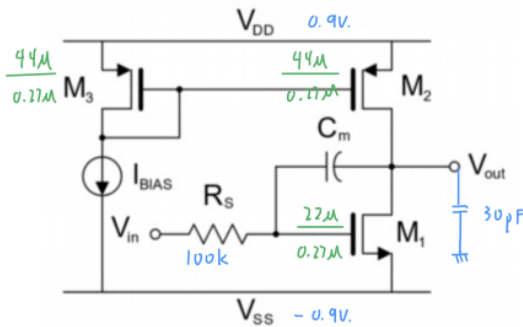

$$GBW = A_{vo} \times f_{p1} \Rightarrow 1M = 32 \times f_{p1} \quad \underline{f_{p1} = 31.25k}$$

$$f_{p2} \geq \sqrt{3} GBW \quad \underline{f_{p2} \geq \sqrt{3} MHz}$$

$$\omega_{p1} = 2\pi f_{p1} = \frac{-1}{|A_{vo}| R_S C_m} \Rightarrow 196.3125k = \frac{-1}{32 \times 100k \times C_m} \quad \underline{C_m = 1.59pF}$$

$$\omega_{p2} = \frac{-G_m}{C_B} = \frac{-g_{m1}}{30pF} \geq 2\pi \times 1M \times \sqrt{3} \quad \underline{g_{m1} \geq 326 \mu}$$


$$A_{vo} = -G_m R_{out} \quad (\lambda = 0.15)$$

$$= -g_{m1} \times (r_{ds1} \parallel r_{ds2}) = 32 = -g_{m1} \times \frac{1}{2 \times I_D} = 32$$

$$\underline{I_{bias} = 33.95 \mu A = I_D}$$

$$g_{m1} = \sqrt{2 \mu n C_{ox} \frac{W}{L} I_D} \Rightarrow 10.62 \mu = 0.12866 \frac{W}{L} \quad \frac{W}{L_n} = 82.5 = \frac{22 \mu}{0.27 \mu}$$
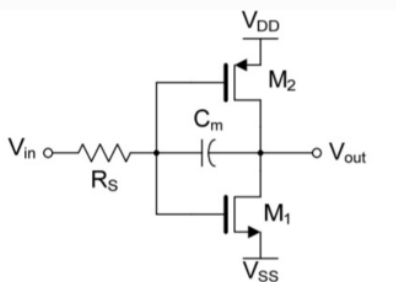
$$\frac{W}{L_p} = \frac{44 \mu}{0.27 \mu}$$



$$GBW = A_{vo} \times f_{p1} \Rightarrow 1M = 32 \times f_{p1} \quad \underline{f_{p1} = 31.25k}$$

$$f_{p2} \geq \sqrt{3} GBW \quad \underline{f_{p2} \geq \sqrt{3} MHz}$$


$$\omega_{p1} = 2\pi f_{p1} = \frac{-1}{|A_{vo}| R_s C_m} \Rightarrow 196.3125k = \frac{-1}{32 \times 100k \times C_m} \quad \underline{C_m = 1.59pF}$$

$$\omega_{p2} = \frac{-G_m}{C_B} = \frac{-g_{m1} + g_{m2}}{30pF} \geq 2\pi \times 1M \times \sqrt{3} \quad \begin{aligned} g_{m1} + g_{m2} &\geq 326 \mu \\ g_{m1} = g_{m2} &= 163 \mu \end{aligned}$$

$$\gamma_L \left(\frac{k_n \left(\frac{W}{L} \right)_n}{k_p \left(\frac{W}{L} \right)_p} \right)^{\gamma_L} = 1 \quad I_D \text{ same}$$

$$k_n \left(\frac{W}{L} \right) = \frac{g_{m1}}{V_{DD} - V_T} \quad \left(\frac{W}{L} \right)_n = \frac{1 \mu}{0.27 \mu} \quad \left(\frac{W}{L} \right)_p = \frac{2 \mu}{0.27 \mu}$$

3.5

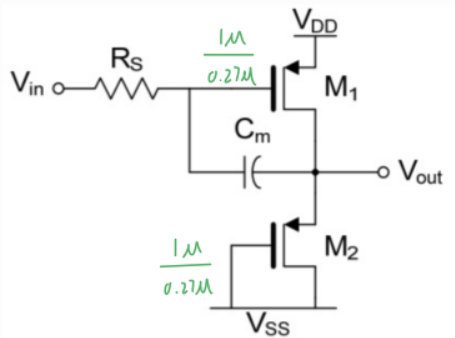


$$GBW = A_{vo} \times f_{p1} \Rightarrow 1 \times f_{p1} \quad \underline{f_{p1} = 1MHz}$$

$$f_{p2} \geq \sqrt{3} GBW \quad \underline{f_{p2} \geq \sqrt{3} MHz}$$

$$\omega_{p1} = 2\pi f_{p1} = \frac{-1}{|A_{vo}| R_s C_m} \Rightarrow 3.14M = \frac{-1}{100k \times C_m} \quad \underline{C_m = 3.18pF}$$

$$f_{p2} = \sqrt{3} GBW = \sqrt{3} MHz \times 2\pi = \frac{g_{m1}}{C_B = 30pF} \quad g_{m1} = 326 \mu = g_{m2}$$
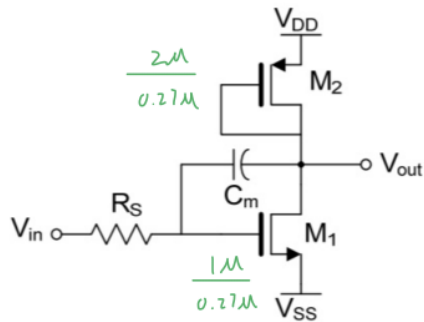
$$\sqrt{2K_P \left(\frac{W}{L} \right)_1 I_D} = \sqrt{2K_P \left(\frac{W}{L} \right)_2 I_D}$$



$$GBW = A_{v0} \times f_{p1} \Rightarrow 1 \times f_{p1}$$

$$f_{p1} = 1 \text{ MHz}$$

$$f_{p2} \geq \sqrt{3} \text{ GBW}$$

$$f_{p2} \geq \sqrt{3} \text{ MHz}$$

$$\omega_{p1} = 2\pi f_{p1} = \frac{-1}{|A_{v0}| R_S C_m} \Rightarrow 3.14 \text{ M} = \frac{-1}{100k \times C_m} \quad \underline{C_m = 3.18 \text{ pF}}$$

$$f_{p2} = \sqrt{3} \text{ GBW} = \sqrt{3} \text{ MHz} \times 2\pi = \frac{g_{m1}}{C_B = 30 \text{ pF}} \quad g_{m1} = 326 \mu = g_{m2}$$

$$\sqrt{2k_p \left(\frac{W}{L}\right)_1 I_D} = \sqrt{2k_p \left(\frac{W}{L}\right)_2 I_D}$$

$$\frac{W}{L} = \frac{5\mu}{0.27\mu} \Rightarrow \text{get } I_D$$