

# 24 Fall ECEN 704: VLSI Circuit Design

## Design Pre-lab Report

### Lab9: Two-Stage Miller Operational Amplifier

Name: Yu-Hao Chen

UIN:435009528

Section:601

Professor: Aydin Karsilayan

TA: Troy Buhr

$A_{v0}$	> 50 dB	> 316
CMRR	> 60 dB	> 1000
GBW	> 2 MHz	
PM	> 45°	
Output Swing (peak-to-peak)	> 1 V	
Load Capacitor	30 pF	
Load Resistor	$\infty$ (open circuit)	
Power Dissipated	< 500 $\mu$ W (including bias current source)	
Power Supply	$V_{DD} = -V_{SS} = 0.9$ V	

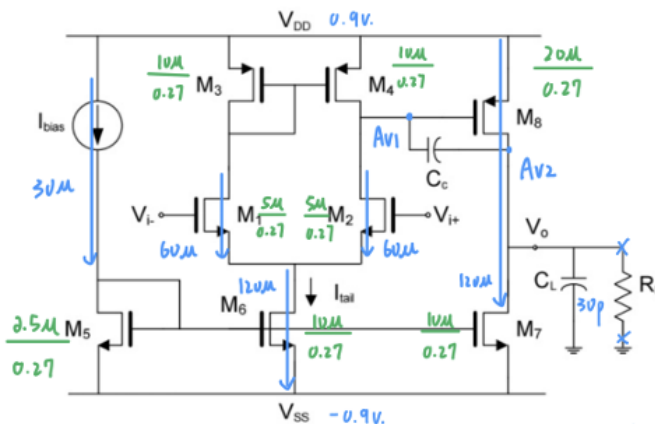


Figure 9-3: Two-Stage Miller op-amp

$$n\lambda = 0.146 \quad p\lambda = 0.183$$

$$A_{v0} = g_{m1} (r_{ds2} \parallel r_{ds4}) g_{m8} (r_{ds7} \parallel r_{ds8})$$

$$g_{m1} = 648.91 \mu \quad g_{m8} = \sqrt{2 \cdot 10 \mu \text{pox} \cdot \frac{W}{L}_8} = 908.82 \mu$$

$$r_{ds2} = \frac{1}{\lambda \cdot I_D} = 114k \quad r_{ds4} = 91k \quad \boxed{50.6k}$$

$$r_{ds7} = 57k \quad r_{ds8} = 45k \quad \boxed{25.14k}$$

$$A_{v0} = 750.2$$

$$A_{CM} = -\frac{1}{2r_{ds6} g_{m3}} = 1.932m \quad g_{m3} = 454 \mu$$

$$CMRR = \frac{A_{v0}}{A_{CM}} = 388k$$

$$WGBW = \frac{g_{m1}}{C_c} = \frac{648.91 \mu}{C_c} > 2MHz \quad C_c < 3.244 \times 10^{-10}$$

$$WGBW = 2.595M \quad C_c = 250pF$$

$$PM = 90^\circ - \tan^{-1} \frac{W_{GBW}}{\omega_{p2}} - \tan^{-1} \frac{W_{GBW}}{\omega_z}$$


$$\omega_{p2} = \frac{-g_{m8}}{C_L} = 30.2M \quad \omega_z = \frac{g_{m8}}{C_C} = 3.63M$$

$$PM = 90^\circ - 4.91^\circ - 35.5^\circ = 49.59$$

$$\text{Swing: } -0.9 + V_{eff7} \sim 0.9 - V_{eff8} = -0.716 \sim 0.64$$

$$\sqrt{\frac{2ID}{K_n \left(\frac{W}{L}\right)_7}} = 0.189 \quad \sqrt{\frac{2ID}{K_p \left(\frac{W}{L}\right)_8}} = 0.26$$
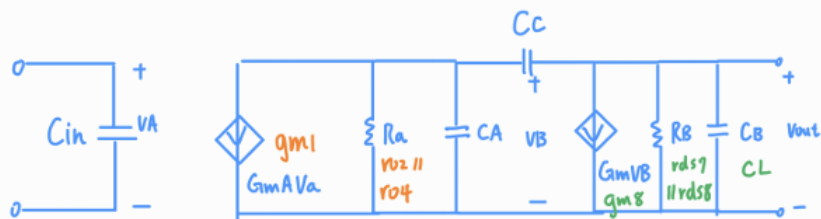
$$\text{Power: } 1.8 \times (30\mu + 2I_{tail}) = 486W$$



$$\omega_{p1} = \frac{-1}{G_{mB} R_B C_C R_A} = \frac{-1}{g_{m8} (r_{o7} || r_{o8}) C_C (r_{o2} || r_{o4})} = \frac{-1}{|A_{V2}| C_C R_A}$$

$$\omega_{p2} = \frac{-G_{mB}}{C_B} = \frac{-g_{m8}}{C_L}$$

$$\omega_z = \frac{G_{mB}}{C_C} = \frac{g_{m8}}{C_C}$$

$$W_{GBW} = \frac{G_{mA}}{C_C} = \frac{g_{m1}}{C_C}$$

